



# POWER ELECTRONICS II


ASSIGNMENT 01

Name: Keshav Gupta

Faculty No. 21EEB176

Enrolment No. GJ8949

Course Code: EEC3210

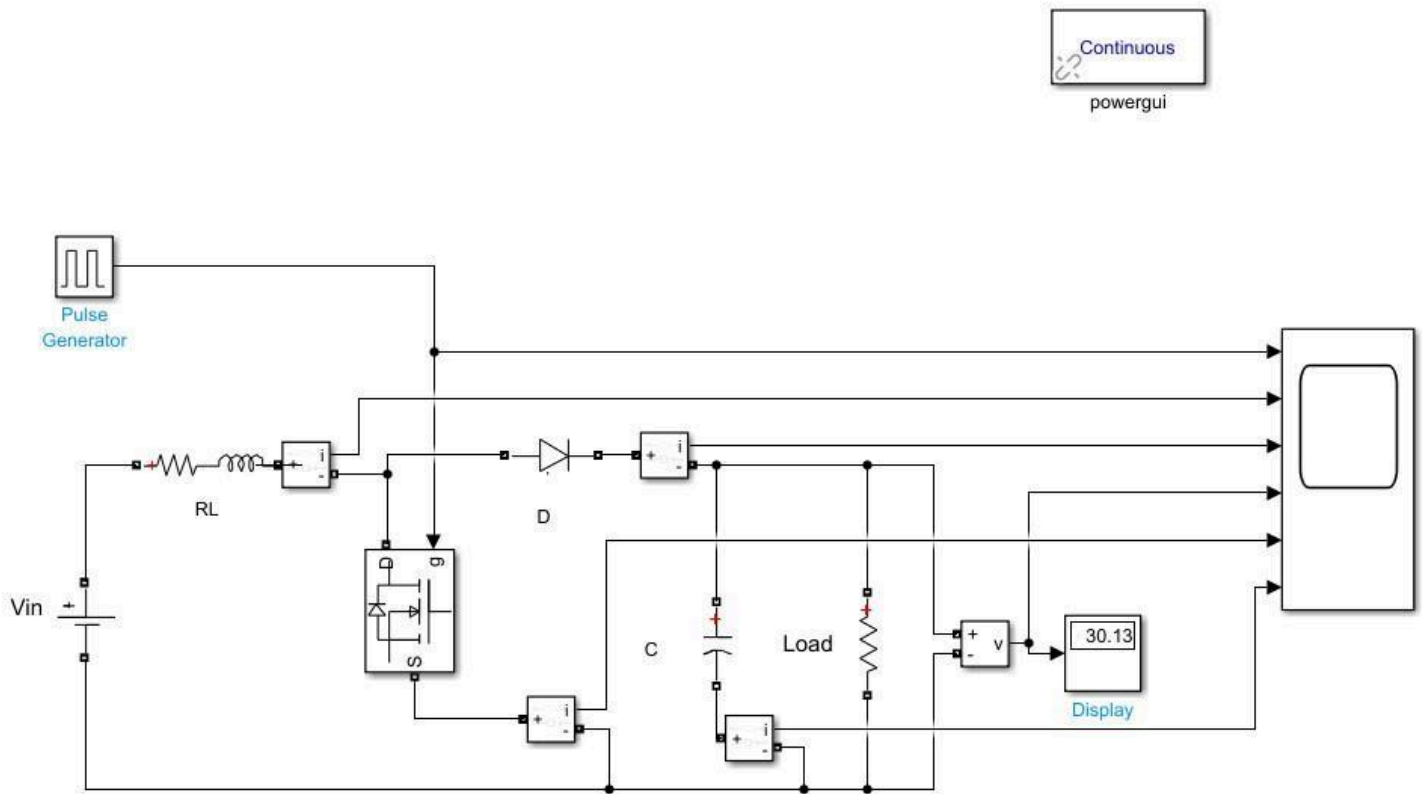

BOOST CONVERTER


**CIRCUIT MODEL**

## CONTINUOUS CONDUCTION MODE


$R=100\ \Omega$      $C=400\ \mu\text{F}$      $V_{in}=12\ \text{V}$      $f=100\text{KHz}$

### # WAVEFORMS:


1) For  $L=2\text{mH}$  and  $D=0.2$

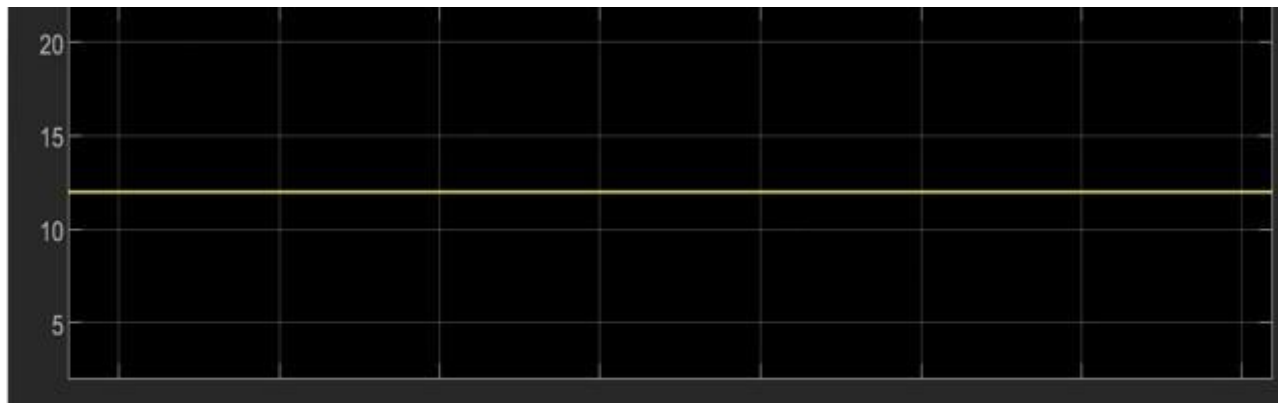


Input Voltage

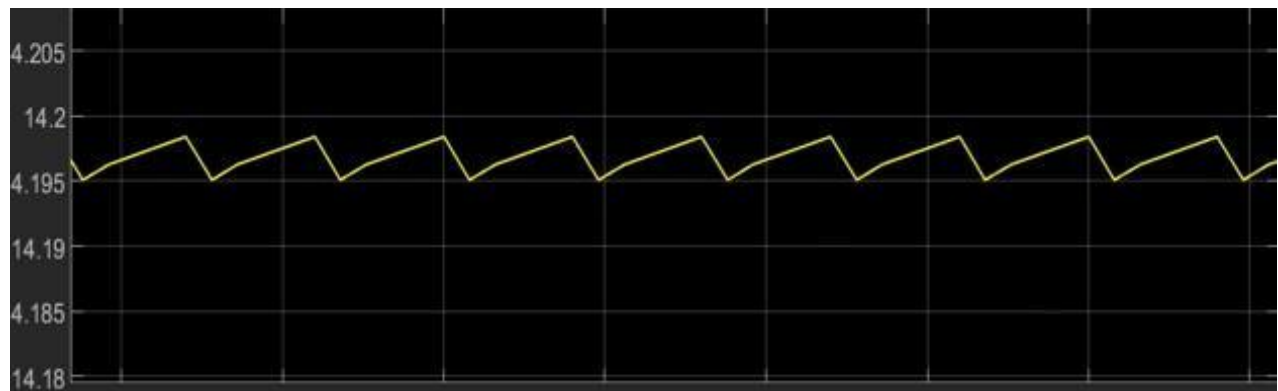


Output Voltage

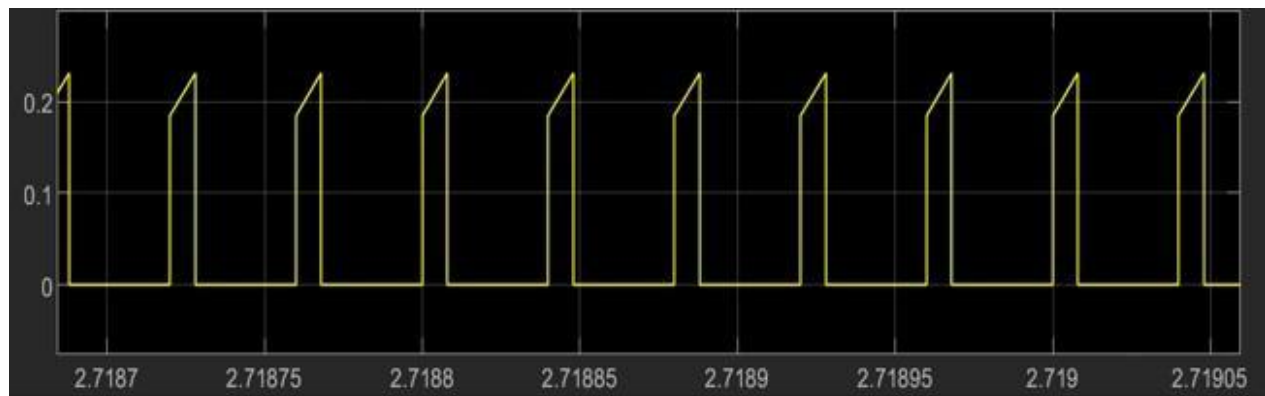


Switch Current

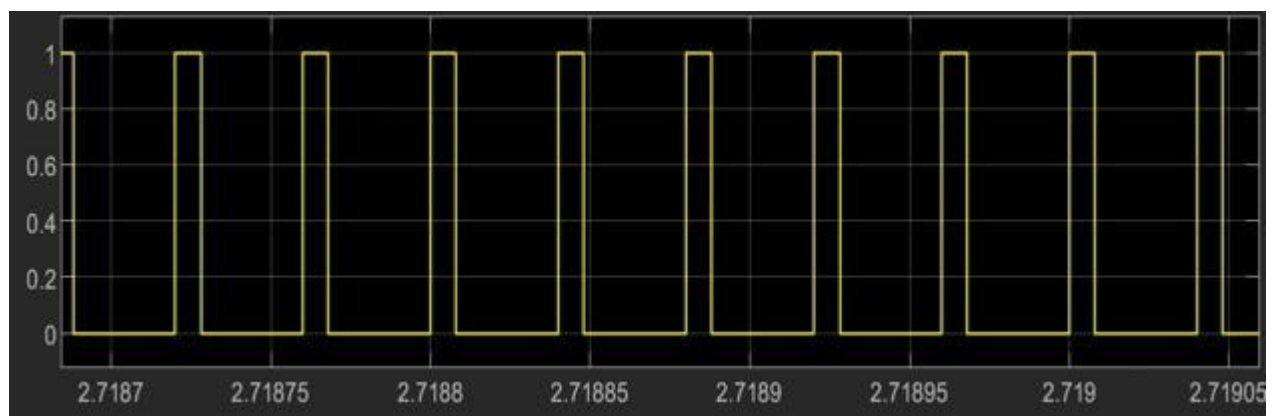

Clock Pulse

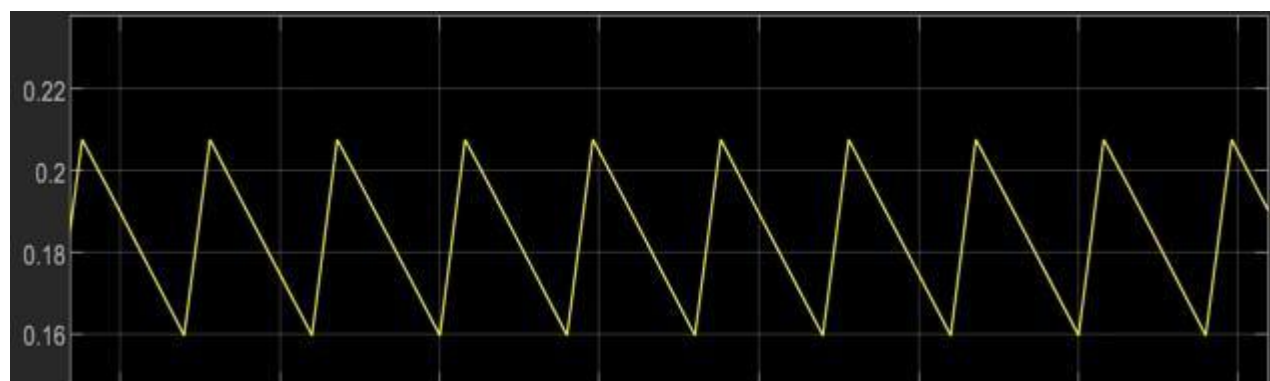


Inductor Current

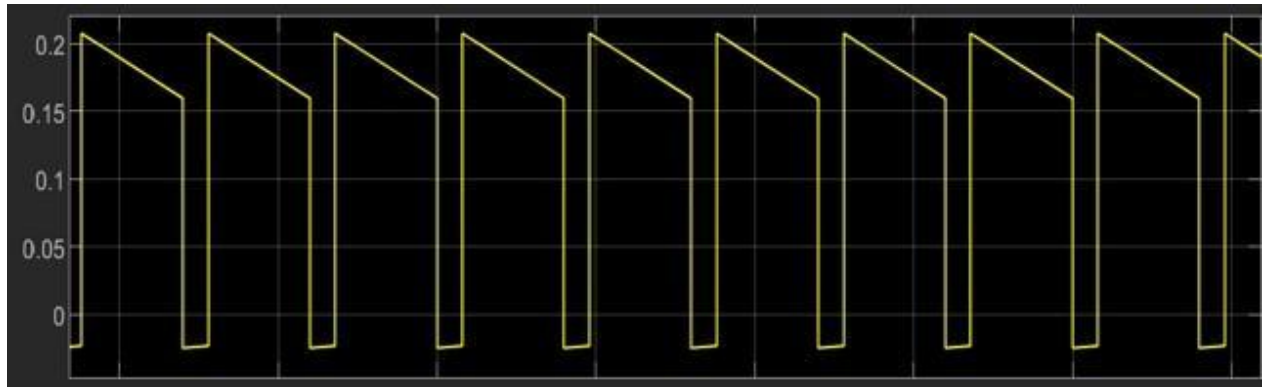


Diode Current


2) For  $L=4\text{mH}$  and  $D=0.4$

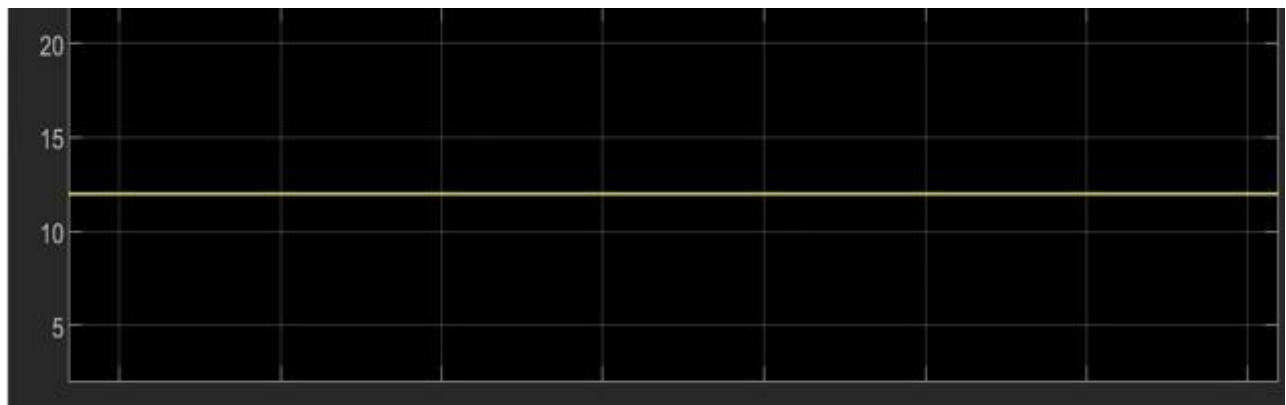


Input Voltage

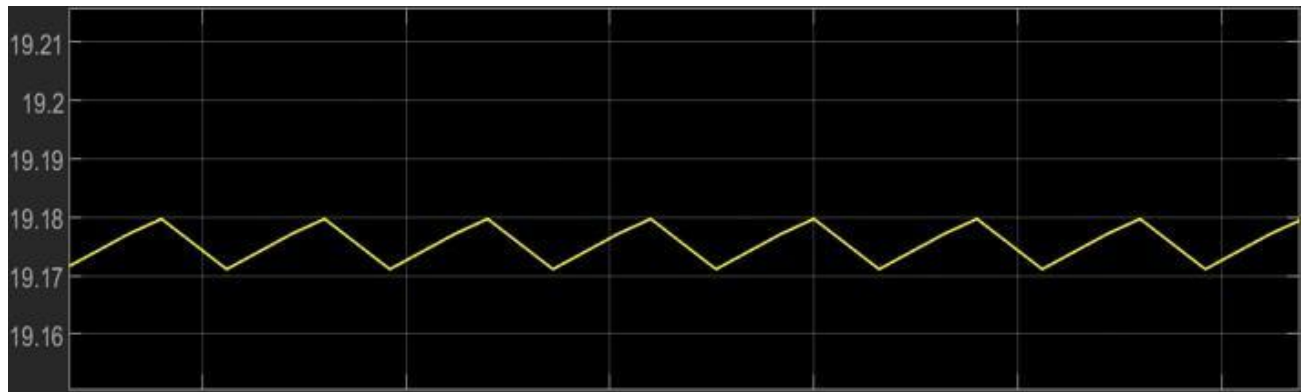


Output Voltage

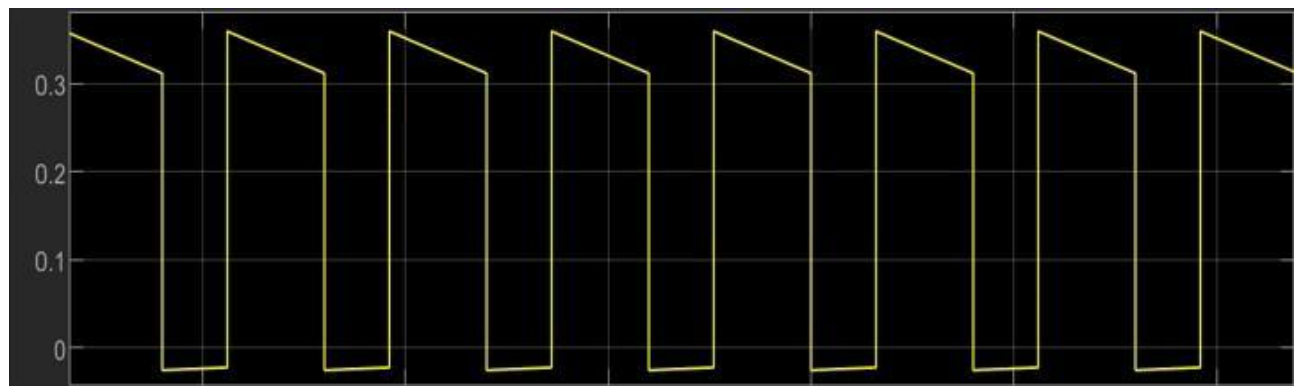


Diode Current

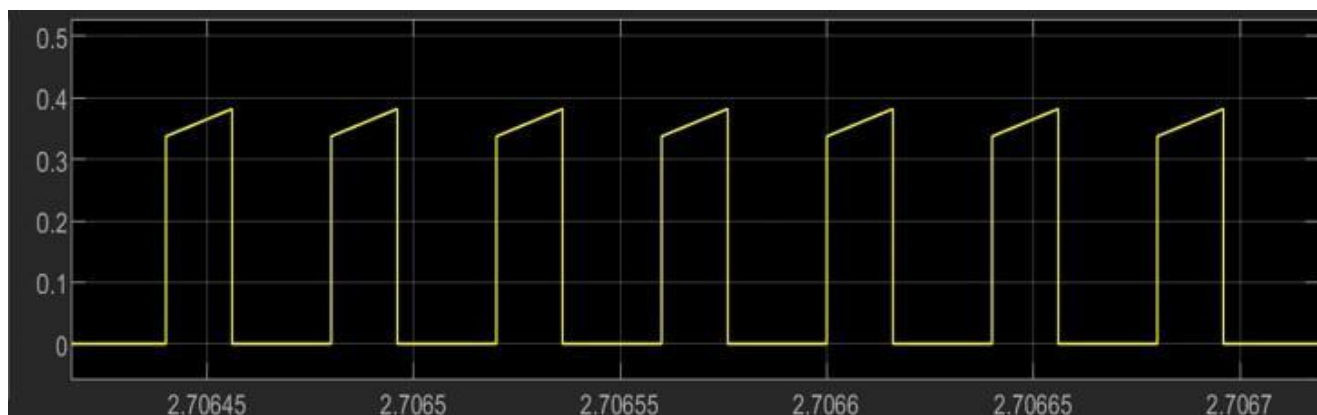

Switch Current

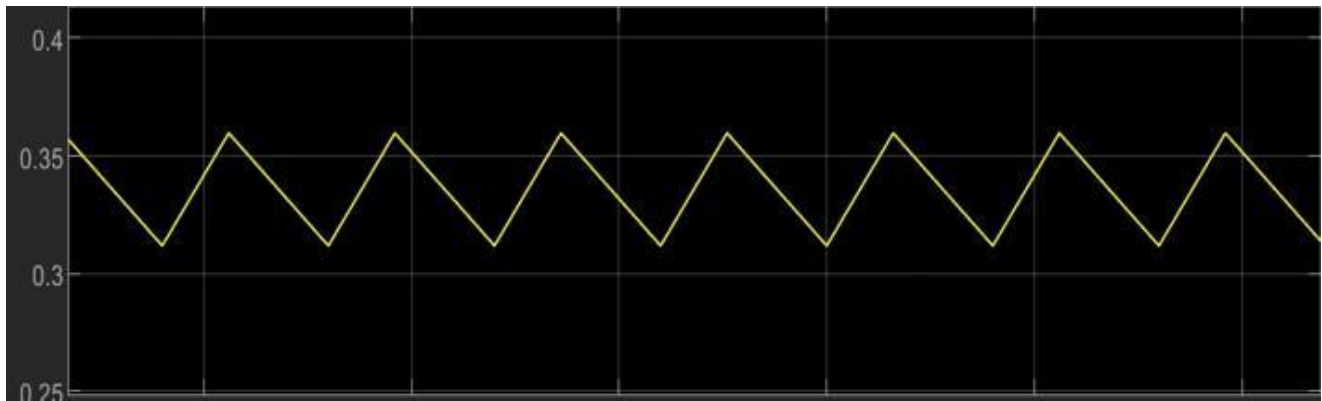

Inductor Current

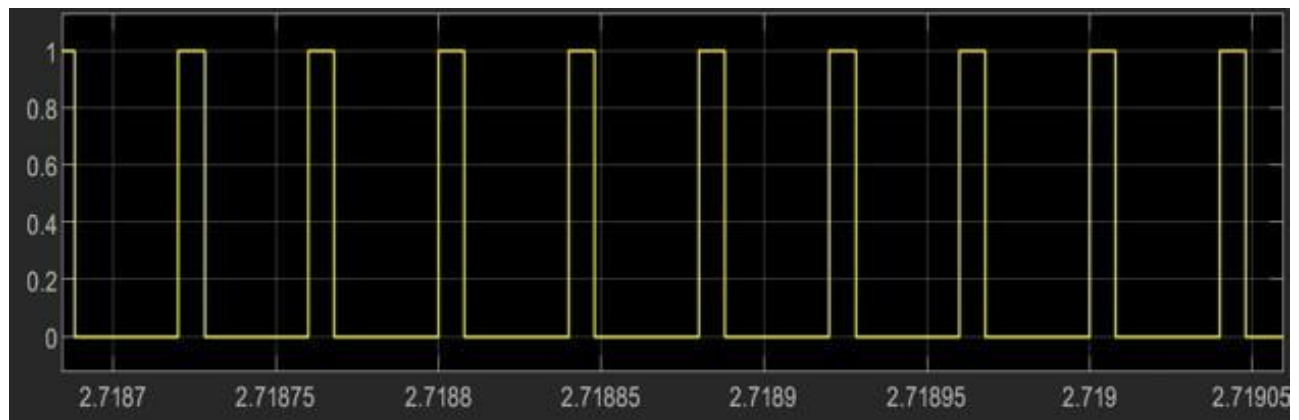


Clock Pulse

## DISCONTINUOUS CONDUCTION MODE


$R=100\ \Omega$      $C=100\ \mu\text{F}$      $V_{in}=12\ \text{V}$      $f=100\text{KHz}$

### # WAVEFORMS:

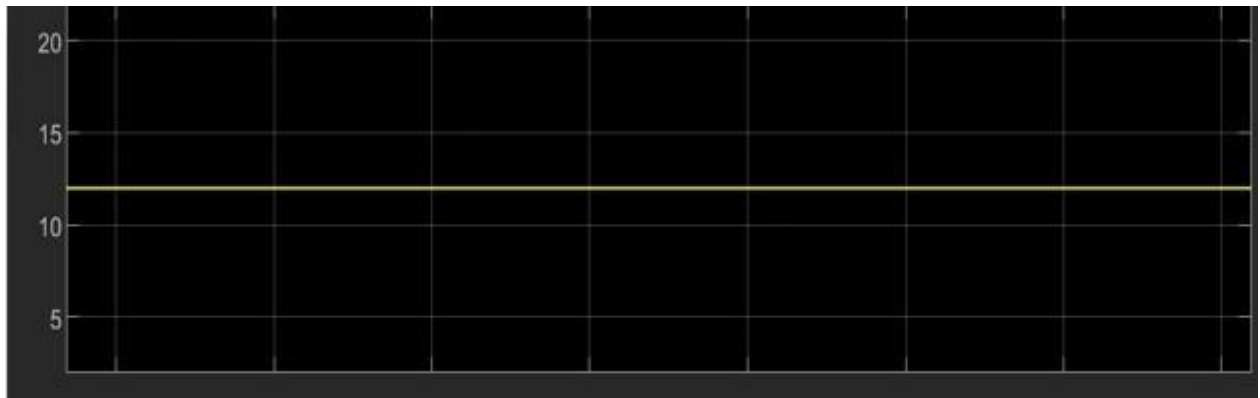- 1) For  $L=20\ \mu\text{H}$  and  $D=0.2$




Input Voltage

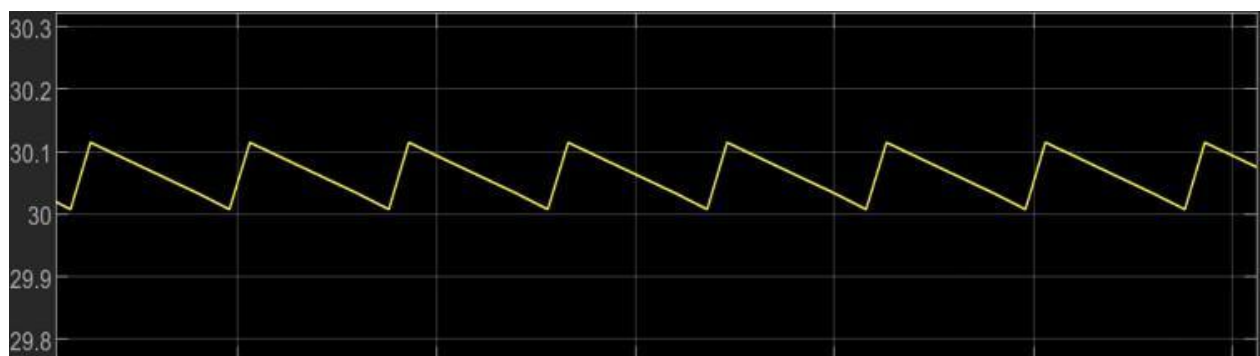

Output Voltage



Diode Current

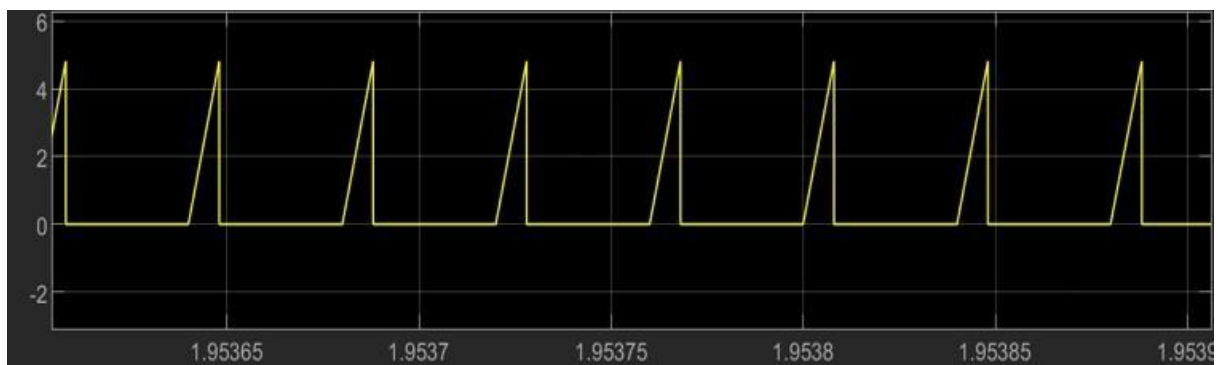




Switch current




### Inductor Current

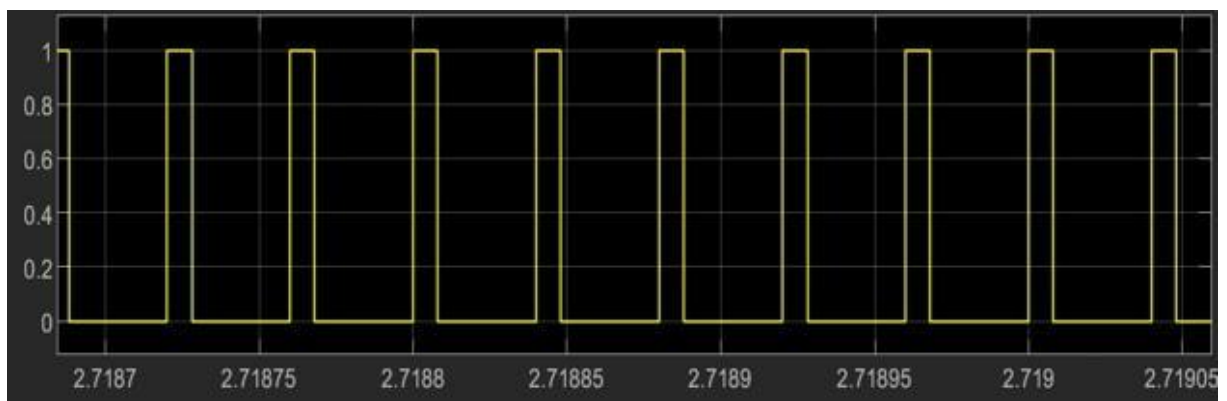

Clock Pulse


2) For  $L=40\mu\text{H}$  and  $D=0.4$

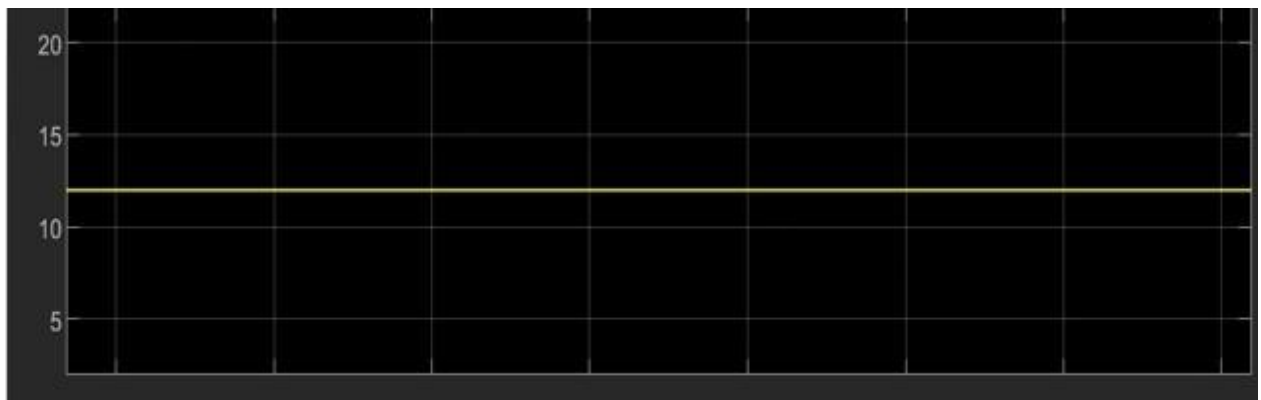


Input Voltage




Diode Current

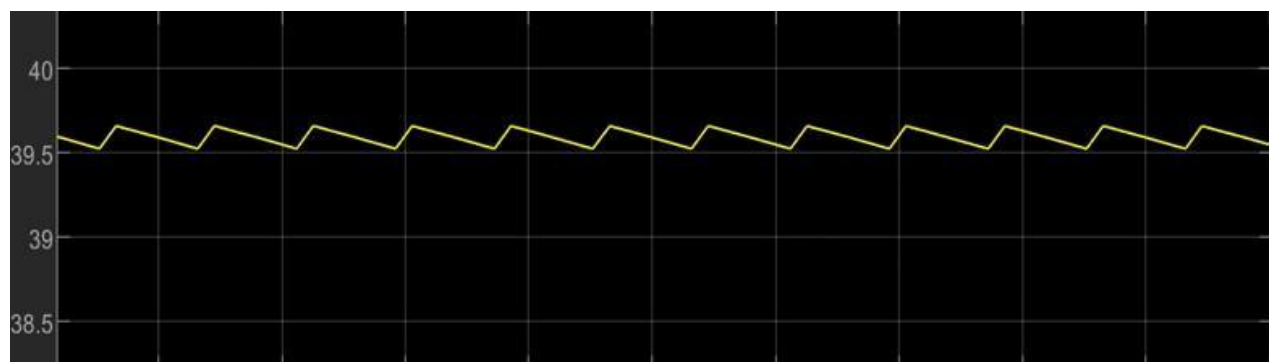


Output Voltage

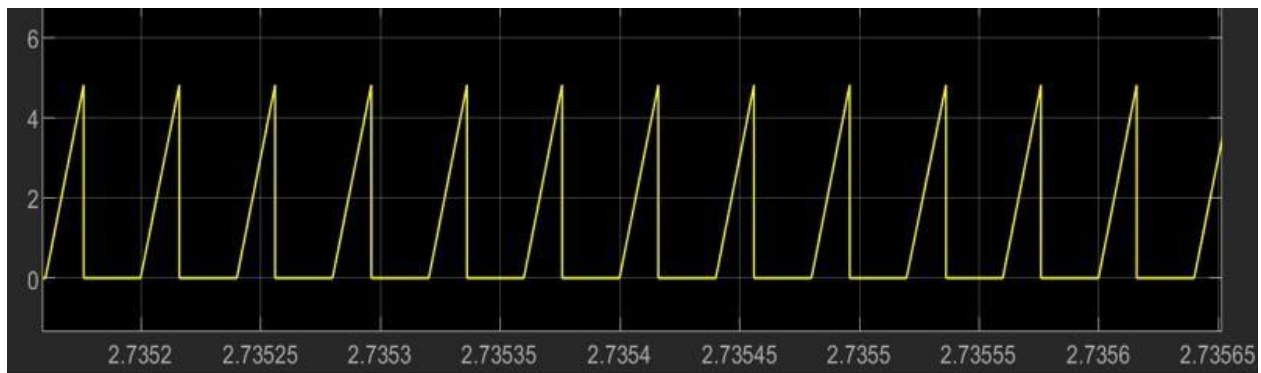

Switch Current

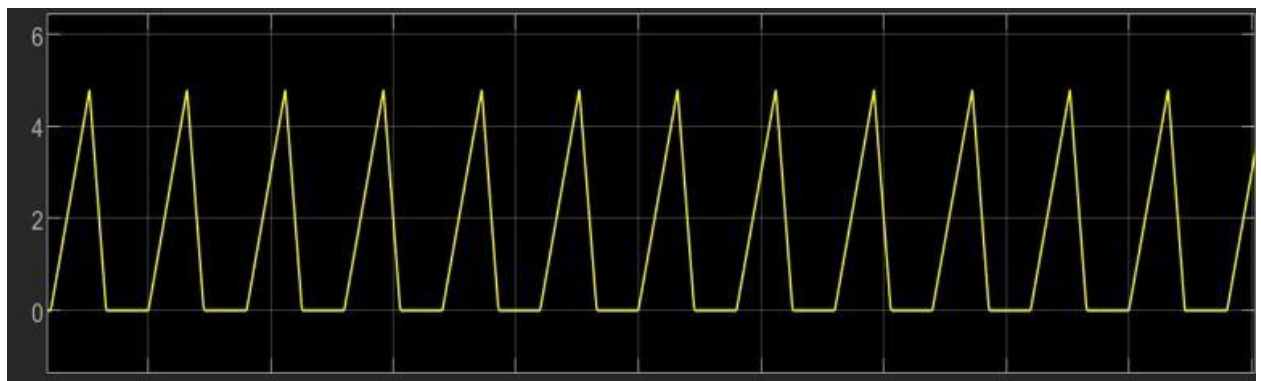

Inductor Current

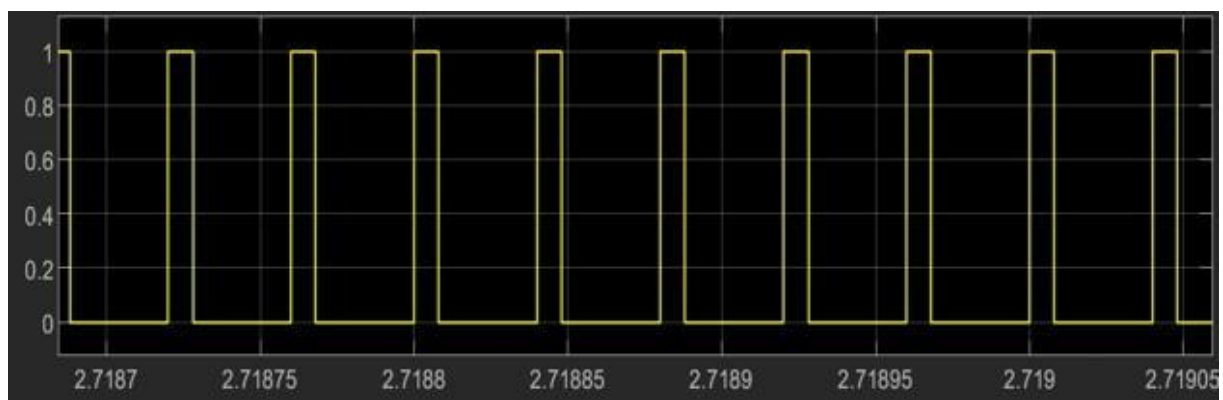

Clock Pulse

